


CircuitJS
Ohm's Law using CircuitJS Simulator - Assignment

Assignment1:

1. In the same circuit, change the resistor value from 1K ohms to 10K Ohms

Tips:

To change the value of any component, select the component and right click and select edit option to change the values.

 

Assignment2:

1. Do the circuit connection as shown in the image, i.e. use both A and B power supply in the circuit
2. Keep the resistor value as 10K Ohms
3. Calculate the current (in mA) flowing through the circuit.

