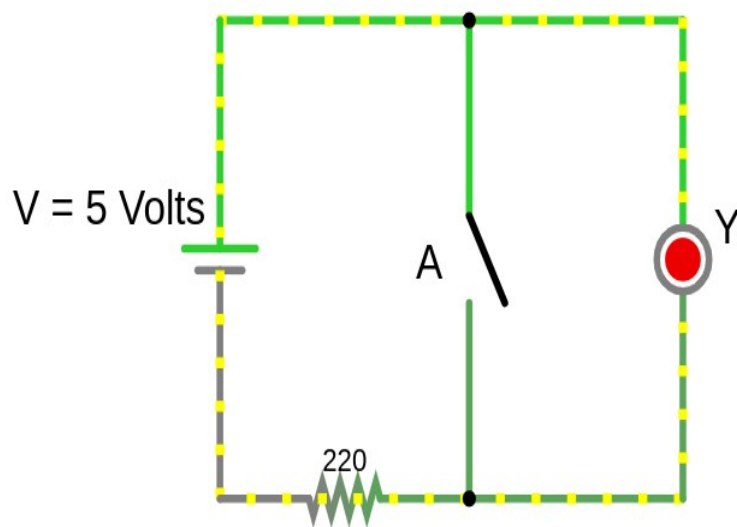


CircuitJS
NOT Gate – Assignment

Assignment 1:

1. Using the switch and LED circuit, verify the **NOT** gate truth table

NOT gate with switch and LED



NOT Gate Truth Table

A	Y
0	0
1	1