

Simple AC Circuits

Spoken Tutorial Project

<https://spoken-tutorial.org>

National Mission on Education through ICT

Script: Dr. Jagdish Kaur
Narration: Amardeep Kaur
DAV College, Amritsar

21 July 2024



Learning Objectives



Learning Objectives

We will learn to,



Learning Objectives

We will learn to,

- ▶ **Build simple AC circuits**



Learning Objectives

We will learn to,

- ▶ Build simple AC circuits
- ▶ Find the phase relation between voltage and current for different AC circuits



Learning Objectives

- ▶ Calculate capacitive reactance and inductive reactance of the circuits



System Requirement



System Requirement

► Windows 11



System Requirement

- ▶ **Windows 11**
- ▶ **Google Chrome v123.0.63**



Prerequisites



Prerequisites

Learners should be familiar with topics in,



Prerequisites

Learners should be familiar with topics in,

▶ **Basic science**



Prerequisites

Learners should be familiar with topics in,

- ▶ Basic science
- ▶ **Simple AC Components**



Alternating Current



Alternating Current

- ▶ Magnitude of AC current changes continuously with time, and its direction reverses periodically



Alternating Current

- ▶ Alternating Current can be represented by Sine or Cosine curve



Alternating Current

- ▶ Alternating Current can be represented by Sine or Cosine curve
- ▶ $I = I_o \sin \omega t$



Alternating Current

- ▶ Alternating Current can be represented by Sine or Cosine curve
- ▶ $I = I_o \sin \omega t$
- ▶ $I = I_o \cos \omega t$



Capacitive Reactance

► Capacitive reactance (X_C)



Capacitive Reactance

- ▶ **Capacitive reactance (X_C)**
- ▶ **It is the opposition offered by a capacitor to the change in current**



Capacitive Reactance

- ▶ Capacitive reactance (X_C)
- ▶ It is the opposition offered by a capacitor to the change in current
- ▶ It depends inversely on the frequency of the ac source



Capacitive Reactance

- ▶ Capacitive reactance (X_C)
- ▶ It is the opposition offered by a capacitor to the change in current
- ▶ It depends inversely on the frequency of the ac source
- ▶ $X_C = \frac{1}{2\pi\nu C}$



Capacitive Reactance

- ▶ Capacitive reactance (X_C)
- ▶ It is the opposition offered by a capacitor to the change in current
- ▶ It depends inversely on the frequency of the ac source
- ▶ $X_C = \frac{1}{2\pi\nu C}$
- ▶ Unit of X_C is ohm(Ω)



Inductive Reactance

► Inductive reactance (X_L)



Inductive Reactance

- ▶ Inductive reactance (X_L)
- ▶ It is the opposition offered by an inductor to the change in current



Inductive Reactance

- ▶ Inductive reactance (X_L)
- ▶ It is the opposition offered by an inductor to the change in current
- ▶ It varies directly with the frequency of the ac source



Inductive Reactance

- ▶ Inductive reactance (X_L)
- ▶ It is the opposition offered by an inductor to the change in current
- ▶ It varies directly with the frequency of the ac source
- ▶ $X_L = 2\pi\nu L$



Inductive Reactance

- ▶ Inductive reactance (X_L)
- ▶ It is the opposition offered by an inductor to the change in current
- ▶ It varies directly with the frequency of the ac source
- ▶ $X_L = 2\pi\nu L$
- ▶ **Unit of X_L is ohm(Ω)**



Link for PhET Simulation

- ▶ Please use the given link for the **Circuit construction kit: AC Virtual Lab**

<https://phet.colorado.edu/sims/html/construction-kit-ac-virtual-lab>



Capacitive Reactance

- ▶ The frequency of AC voltage source is 0.5 Hz



Capacitive Reactance

- ▶ The frequency of AC voltage source is 0.5 Hz
- ▶ Capacitance of the capacitor is 0.1 F



Capacitive Reactance

- ▶ The frequency of AC voltage source is 0.5 Hz
- ▶ Capacitance of the capacitor is 0.1 F
- ▶ $X_C = \frac{1}{2\pi\nu C} = \frac{1}{2 \times 3.14 \times 0.5 \times 0.1}$



Capacitive Reactance

- ▶ The frequency of AC voltage source is 0.5 Hz
- ▶ Capacitance of the capacitor is 0.1 F
- ▶ $X_C = \frac{1}{2\pi\nu C} = \frac{1}{2 \times 3.14 \times 0.5 \times 0.1}$
- ▶ $X_C = 3.18 \Omega$



Inductive Reactance

- ▶ The frequency of AC voltage source is 0.5 Hz



Inductive Reactance

- ▶ The frequency of AC voltage source is 0.5 Hz
- ▶ Inductance of the inductor is 5 H



Inductive Reactance

- ▶ The frequency of AC voltage source is 0.5 Hz
- ▶ Inductance of the inductor is 5 H
- ▶ $X_L = 2\pi\nu L = 2 \times 3.14 \times 0.5 \times 5$



Inductive Reactance

- ▶ The frequency of AC voltage source is 0.5 Hz
- ▶ Inductance of the inductor is 5 H
- ▶ $X_L = 2\pi\nu L = 2 \times 3.14 \times 0.5 \times 5$
- ▶ $X_L = 15.7 \Omega$



Series AC Circuits

- ▶ In AC Circuits resistor, capacitor and inductor are connected in series



Series AC Circuits

- ▶ In AC Circuits resistor, capacitor and inductor are connected in series
- ▶ The impedance (Z) is the total opposition to the flow of current in the AC circuit



Series AC Circuits

- ▶ In AC Circuits resistor, capacitor and inductor are connected in series
- ▶ The impedance (Z) is the total opposition to the flow of current in the AC circuit
- ▶ $Z = \sqrt{R^2 + (X_L - X_C)^2}$



Series AC Circuits

For,



Series AC Circuits

For,

▶ LC circuit, $R = 0$,



Series AC Circuits

For,

- ▶ LC circuit, $R = 0$,
- ▶ RC circuit, $X_L = 0$ and



Series AC Circuits

For,

- ▶ LC circuit, $R = 0$,
- ▶ RC circuit, $X_L = 0$ and
- ▶ LR circuit, $X_C = 0$



Series AC Circuits

- ▶ The resistance of the resistor is 10Ω



Series AC Circuits

- ▶ The resistance of the resistor is 10Ω
- ▶ The capacitance is 0.10 F



Series AC Circuits

- ▶ The resistance of the resistor is 10Ω
- ▶ The capacitance is 0.10 F
- ▶ Capacitive reactance, $X_C = 3.18 \Omega$



Series AC Circuits

- ▶ The resistance of the resistor is 10Ω
- ▶ The capacitance is 0.10 F
- ▶ Capacitive reactance, $X_C = 3.18 \Omega$
- ▶ Impedance(Z) = $\sqrt{(R^2 + X_C^2)}$



Series AC Circuits

- ▶ The resistance of the resistor is 10Ω
- ▶ The capacitance is 0.10 F
- ▶ Capacitive reactance, $X_C = 3.18 \Omega$
- ▶ Impedance(Z) = $\sqrt{(R^2 + X_C^2)}$
- ▶ $Z = 4.48 \Omega$



Summary

Using this simulation we,

- ▶ Built simple AC circuits
- ▶ Found the phase relation between voltage and current for different AC circuits
- ▶ Calculated capacitive reactance & inductive reactance of the circuits



Assignment

- ▶ Change the frequency of the AC voltage source to 0.75 hertz and 1.0 hertz
- ▶ Find capacitive reactance and inductive reactance at these frequencies



Assignment

Find the phase relation between voltage and current for:

- ▶ Series LC circuit
- ▶ Series RL circuit



About the Spoken Tutorial Project

- ▶ Watch the video available at https://spoken-tutorial.org/What_is_a_Spoken_Tutorial
- ▶ It summarises the Spoken Tutorial project



About the Spoken Tutorial Project

- ▶ Watch the video available at https://spoken-tutorial.org/What_is_a_Spoken_Tutorial
- ▶ It summarises the Spoken Tutorial project
- ▶ If you do not have good bandwidth, you can download and watch it



Spoken Tutorial Workshops

The Spoken Tutorial Project Team

- ▶ Conducts workshops using spoken tutorials
- ▶ Gives certificates to those who pass an online test
- ▶ For more details, please write to contact@spoken-tutorial.org



Forum questions

- ▶ Questions in THIS Spoken Tutorial?
- ▶ Visit <https://forums.spoken-tutorial.org>
- ▶ Choose the minute and second where you have the question
- ▶ Explain your question briefly
- ▶ The Spoken Tutorial project will ensure an answer

You will have to register to ask questions



Acknowledgements

The Spoken Tutorial project was established by the Ministry of Education, Govt. of India



Thank You!

- ▶ This tutorial is contributed by Dr. Jagdish Kaur and Muskandeeep Kaur from DAV College Amritsar
- ▶ Thank you for joining

