

LCR Series and Parallel Circuits

Spoken Tutorial Project

<https://spoken-tutorial.org>

National Mission on Education through ICT

Script: Dr. Jagdish Kaur
Narration: Amardeep Kaur
DAV College, Amritsar



24 July 2024



Learning Objectives



Learning Objectives

We will learn to,



Learning Objectives

We will learn to,

- ▶ **Buid LCR circuits in series and parallel combination**



Learning Objectives

We will learn to,

- ▶ Build LCR circuits in series and parallel combination
- ▶ Calculate the resonance frequency from the graph and formula



System Requirement



System Requirement

► Windows 11



System Requirement

- ▶ Windows 11
- ▶ Google Chrome v123.0.63



Prerequisites



Prerequisites

Learners should be familiar with topics in,



Prerequisites

Learners should be familiar with topics in,

► **Simple AC circuits**



Resonance Frequency



Resonance Frequency

The frequency at which



Resonance Frequency

The frequency at which

- ▶ Impedance of the LCR circuit becomes minimum
or



Resonance Frequency

The frequency at which

▶ Impedance of the LCR circuit becomes minimum

or

▶ Current in the circuit becomes maximum



Resonance Frequency



Resonance Frequency

- ▶ Resonance frequency(ν) is given by



Resonance Frequency

▶ Resonance frequency(ν) is given by

▶
$$\nu = \frac{1}{2\pi\sqrt{LC}}$$



Link for PhET Simulation

- ▶ Please use the given link for the **Circuit construction kit: AC Virtual Lab**

<https://phet.colorado.edu/en/simulations/circuit-construction-kit-ac-virtual-lab>




LCR Series Circuit

Frequency (Hz)	Current (A)
0.1	0.56
0.12	0.66
0.14	0.74
0.16	0.8
0.18	0.86
0.2	0.89
0.22	0.89
0.24	0.92
0.26	0.88
0.28	0.86
0.3	0.83
0.32	0.81
0.34	0.77
0.36	0.73
0.38	0.7
0.4	0.68



LCR Series Circuit

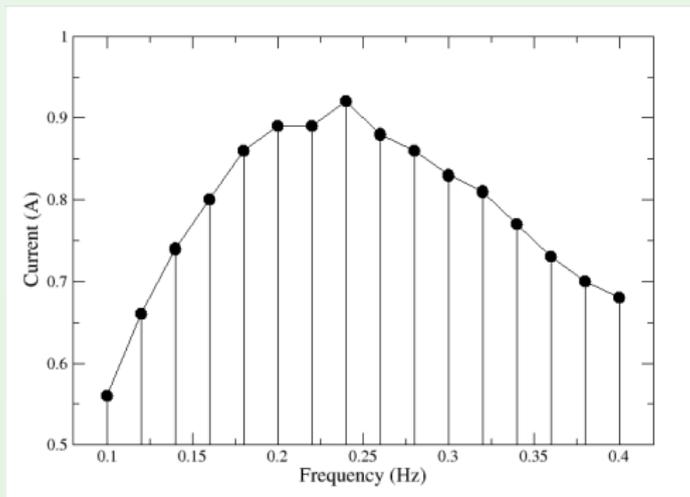

From graph Current has maximum value at 0.24 Hz frequency




LCR Parallel Circuit

Frequency (Hz)	Current (A)
0.1	0.75
0.12	0.7
0.14	0.63
0.16	0.56
0.18	0.52
0.2	0.48
0.22	0.45
0.24	0.44
0.26	0.46
0.28	0.5
0.3	0.54
0.32	0.57
0.34	0.61
0.36	0.63
0.38	0.65
0.4	0.67



LCR Series Circuit

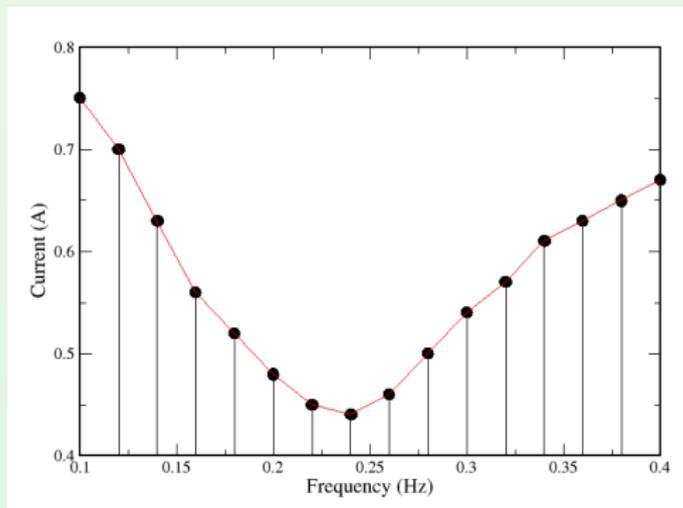

From graph Current has minimum value at 0.24 Hz frequency



Resonance frequency from equation

In LCR series and parallel circuits,



Resonance frequency from equation

In LCR series and parallel circuits,

▶ Inductance, $L = 5 \text{ H}$



Resonance frequency from equation

In LCR series and parallel circuits,

- ▶ Inductance, $L = 5 \text{ H}$
- ▶ Capacitance, $C = 0.1 \text{ F}$



Resonance frequency from equation

In LCR series and parallel circuits,

- ▶ Inductance, $L = 5 \text{ H}$
- ▶ Capacitance, $C = 0.1 \text{ F}$
- ▶ Resonance frequency,

$$\nu = \frac{1}{2\pi\sqrt{5 \times 0.1}}$$

$$\nu = 0.225 \text{ Hz}$$



Summary

Using this simulation we have,

- ▶ Built LCR circuits in series and parallel combination
- ▶ Calculated the resonance frequency from the graph and formula



Assignment 1

- ▶ Change the inductance to 7 H and capacitance to 0.2 F
- ▶ Calculate the resonance frequency



Assignment 2

- ▶ Change the resistance values to 5 ohms and 15 ohms
- ▶ Find the variation of current with frequency



Spoken Tutorial Project

- ▶ The video at the following link summarises the Spoken Tutorial Project https://spoken-tutorial.org/What_is_a_Spoken_Tutorial



Spoken Tutorial Project

- ▶ The video at the following link summarises the Spoken Tutorial Project https://spoken-tutorial.org/What_is_a_Spoken_Tutorial
- ▶ Please download and watch it



Spoken Tutorial Workshops

The Spoken Tutorial Project Team

- ▶ Conducts workshops using spoken tutorials
- ▶ Gives certificates to those who pass an online test
- ▶ For more details, please write to contact@spoken-tutorial.org



Forum questions

- ▶ Questions in THIS Spoken Tutorial?
- ▶ Visit <https://forums.spoken-tutorial.org>
- ▶ Choose the minute and second where you have the question
- ▶ Explain your question briefly
- ▶ The Spoken Tutorial project will ensure an answer

You will have to register to ask questions



Acknowledgements

The Spoken Tutorial project was established by the Ministry of Education, Govt. of India



Thank You!

- ▶ This tutorial is contributed by Dr. Jagdish Kaur and Amardeep Kaur from DAV College Amritsar
- ▶ Thank you for joining

