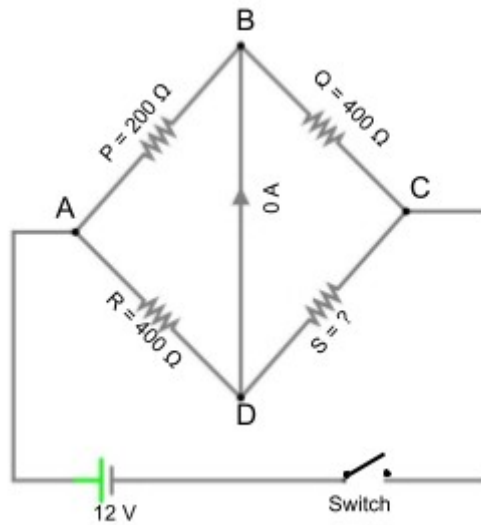


CircuitJS  
Wheatstone Bridge – Assignment

Assignment:



1. Change the values of resistor P to 60 ohms, resistor Q to 150 ohms, resistor R to 300 ohms.
2. Use the **Wheatstone Bridge** balance condition formula to find the value of resistor S